

## **Test Plan**

Verify That:

1. C becomes 0 after reset is asserted.
2. When opcode is 2'b00 the sum of A and B appears on C after one clock cycle.
  - a. Must be two's complement
3. When opcode is 2'b01 the difference of A and B appears on C after clock cycle.
  - a. Must be two's complement
4. When opcode is 2'b10 the bitwise inverse of A appears on C after one clock cycle.
5. When opcode is 2'b11 the reduction OR of B appears on C after one clock cycle.

## **Procedure**

The fact that there were only 11 input bits made it possible to exhaustively test all 2048 input combinations. For each input combination, the result was calculated and then compared to the output of the ALU (C). For all input combinations the ALU worked performed properly.

However, it is not possible in most cases to exhaustively test all input combinations to a circuit. So it might be interesting to consider which directed tests I might have performed to ensure that the circuit was working correctly.

To prove that the reset is functioning properly, we would want to ensure that the register resets to zero when the reset is asserted regardless of which opcode or inputs were applied. My directed tests would have included asserting the reset while applying several randomly chosen opcode and inputs and demonstrating that the circuit operates properly.

For add and subtract I would have tried a variety of random combinations of positive and negative numbers. I would also increment and decrement by one through the entire space. Then I may also have incremented by powers of 2 (2, 4, 8, etc.). To get a good feel that each of the bits in the adder was individually responsive.

Bitwise operation are the easiest to vet since each bit is operated on individually. The correct functionality can be shown using two tests: all ones and all zeros. Other directed tests could include rotating a single one or single zero through each of the inputs. This help demonstrate that each of the bits is independent of the other bits. It would also be important to show that the result is independent of the B input. This would be done by cycling different patterns through B while performing additional tests on B.

For the reduction OR I would have rotated a single one through each of the inputs as well as have tested all ones and all zeros. Then I would have tested several inputs on A to show that the result is independent of A.

## ALU Test-bench Code

```
`default_nettype none
`timescale 1ns/100ps

module alu_testbench ();

    reg clk;
    wire reset;
    wire [1:0] Opcode;
    wire signed [3:0] A;
    wire signed [3:0] B;
    wire signed [4:0] C;

    reg signed [10:0] test_vector;
    reg [4:0] expected_result;
    integer errors;

    always begin
        #10 clk = !clk;
    end

    ALU_4_bit ALU(clk,
                  reset,
                  Opcode,
                  A, B, C );

    assign A = test_vector[3:0];
    assign B = test_vector[7:4];
    assign reset = test_vector[8];
    assign Opcode = test_vector[10:9];

    initial begin
        $display("Starting Testbench:");
        clk = 0;
        test_vector = 11'b1111111111;
        errors = 16'd0;
        forever begin
            @ (negedge clk)
                //Update Test Vector
                test_vector = test_vector + 1'b1;
                //Wait to allow wire value to propagate
                #1 //ns
                //Define Expected Results based on Current Inputs
                if(reset) begin
                    expected_result = 5'b0;
                end else begin
                    case (Opcode)
                        2'b00: expected_result = A + B;
                        2'b01: expected_result = A - B;
                        2'b10: expected_result = ~A;
```

```

        2'b11: expected_result = |B;
    endcase
end

@ (posedge clk)

#1 //ns

if(expected_result != C) begin
    errors = errors + 1;
    $display("Error @ time %d: Reset: %d Opcode: %d A: %d B: %d C: %d
Expected Result: %d", $time, reset, Opcode, A, B, C, expected_result);
end

if(test_vector == 11'b1111111111) begin
    $display("Test Complete: Found %d Errors", errors);
    $finish;
end

end
end

endmodule

```

### Transcript Window Output (Working)

```

do testbench.do
# vsim -novopt alu_testbench
# Refreshing
/net/fpga1/users/joshuas2/ECEn620/Assignments/Assignment1/work.alu_testbn
ch
# Loading work.alu_testbench
# Refreshing
/net/fpga1/users/joshuas2/ECEn620/Assignments/Assignment1/work.ALU_4_bit
# Loading work.ALU_4_bit
# Starting Testbench:
# Test Complete: Found      0 Errors
# ** Note: $finish  :
/net/fpga1/users/joshuas2/ECEn620/Assignments/Assignment1/alu_testbench.v(
65)

# Time: 40971 ns Iteration: 0 Instance: /alu_testbench

```

## Transcript Window Output (Not Working) Changed ~A to A

```
o testbench.do

# vsim -novopt alu_testbench
# Refreshing
/net/fpga1/users/joshuas2/ECEn620/Assignments/Assignment1/work.alu_testbench
# Loading work.alu_testbench
# Refreshing /net/fpga1/users/joshuas2/ECEn620/Assignments/Assignment1/work.ALU_4_bit
# Loading work.ALU_4_bit
# Starting Testbench:

# Error @ time      20511: Reset: 0 Opcode: 2 A: 0 B: 0 C: 0 Expected Result: 31
# Error @ time      20531: Reset: 0 Opcode: 2 A: 1 B: 0 C: 1 Expected Result: 30
# Error @ time      20551: Reset: 0 Opcode: 2 A: 2 B: 0 C: 2 Expected Result: 29
# Error @ time      20571: Reset: 0 Opcode: 2 A: 3 B: 0 C: 3 Expected Result: 28
# Error @ time      20591: Reset: 0 Opcode: 2 A: 4 B: 0 C: 4 Expected Result: 27
# Error @ time      20611: Reset: 0 Opcode: 2 A: 5 B: 0 C: 5 Expected Result: 26
# Error @ time      20631: Reset: 0 Opcode: 2 A: 6 B: 0 C: 6 Expected Result: 25
# Error @ time      20651: Reset: 0 Opcode: 2 A: 7 B: 0 C: 7 Expected Result: 24
# Error @ time      20671: Reset: 0 Opcode: 2 A: -8 B: 0 C: -8 Expected Result: 7
# Error @ time      20691: Reset: 0 Opcode: 2 A: -7 B: 0 C: -7 Expected Result: 6
...

#Error @ time      25411: Reset: 0 Opcode: 2 A: 5 B: -1 C: 5 Expected Result: 26
# Error @ time      25431: Reset: 0 Opcode: 2 A: 6 B: -1 C: 6 Expected Result: 25
# Error @ time      25451: Reset: 0 Opcode: 2 A: 7 B: -1 C: 7 Expected Result: 24
# Error @ time      25471: Reset: 0 Opcode: 2 A: -8 B: -1 C: -8 Expected Result: 7
# Error @ time      25491: Reset: 0 Opcode: 2 A: -7 B: -1 C: -7 Expected Result: 6
# Error @ time      25511: Reset: 0 Opcode: 2 A: -6 B: -1 C: -6 Expected Result: 5
# Error @ time      25531: Reset: 0 Opcode: 2 A: -5 B: -1 C: -5 Expected Result: 4
# Error @ time      25551: Reset: 0 Opcode: 2 A: -4 B: -1 C: -4 Expected Result: 3
# Error @ time      25571: Reset: 0 Opcode: 2 A: -3 B: -1 C: -3 Expected Result: 2
# Error @ time      25591: Reset: 0 Opcode: 2 A: -2 B: -1 C: -2 Expected Result: 1
# Error @ time      25611: Reset: 0 Opcode: 2 A: -1 B: -1 C: -1 Expected Result: 0

# Test Complete: Found      256 Errors

# ** Note: $finish :
/net/fpga1/users/joshuas2/ECEn620/Assignments/Assignment1/alu_testbench.v(65)

# Time: 40971 ns Iteration: 0 Instance: /alu_testbench
```